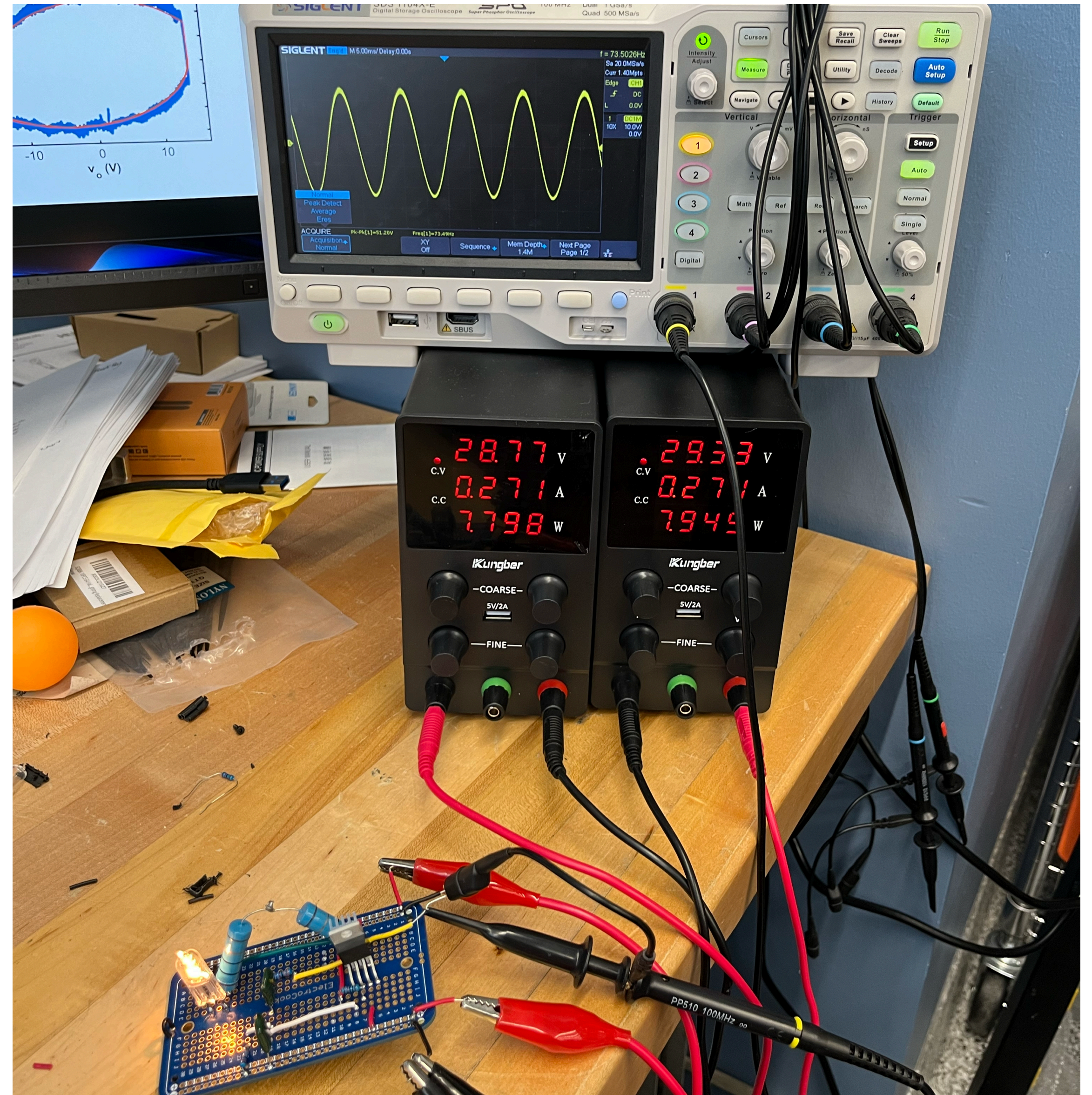


# Nonlinear Analysis of the Wein Bridge Oscillator Circuit

18.385 Spring 2024

Ronak Roy

May 08, 2024



# Electronic Circuits Primer

 Resistor  $v = Ri$


 Capacitor  $\frac{dv}{dt} = \frac{1}{C}i$

 Inductor  $v = L\frac{di}{dt}$

$$v = Ri \Leftrightarrow V(s) = RI(s) \Rightarrow Z_R = R$$

$$\frac{dv}{dt} = \frac{1}{C}i \Leftrightarrow V(s) = \frac{1}{sC}I(s) \Rightarrow Z_C = \frac{1}{sC}$$
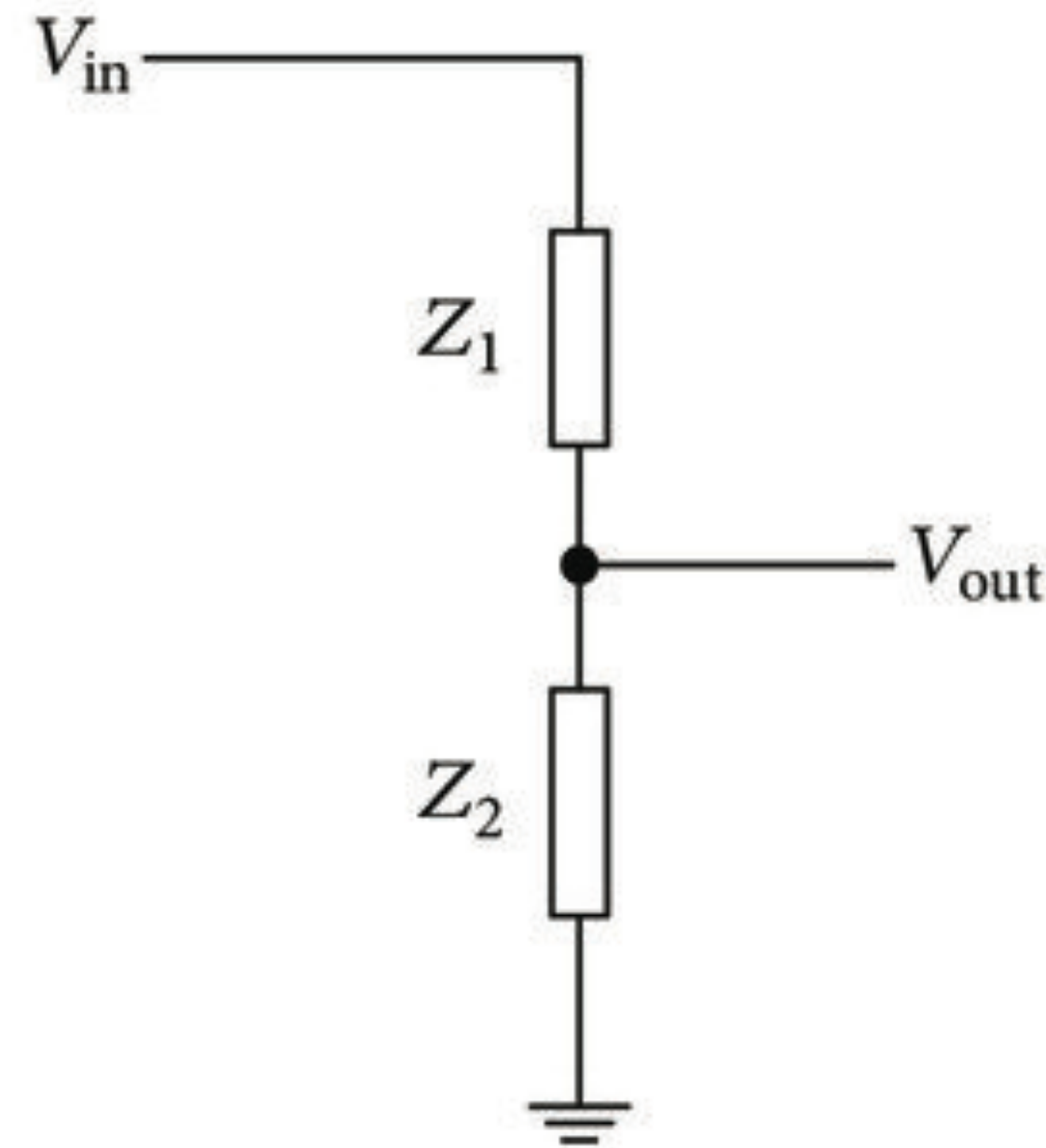
$$v = L\frac{di}{dt} \Leftrightarrow V(s) = sLI(s) \Rightarrow Z_L = sL$$




$$V_{source} = V_{in} - V_{out} = V_{in} \frac{Z_1}{Z_1 + Z_2}$$

$$V_{load} = V_{out} = V_{in} \frac{Z_2}{Z_1 + Z_2}$$
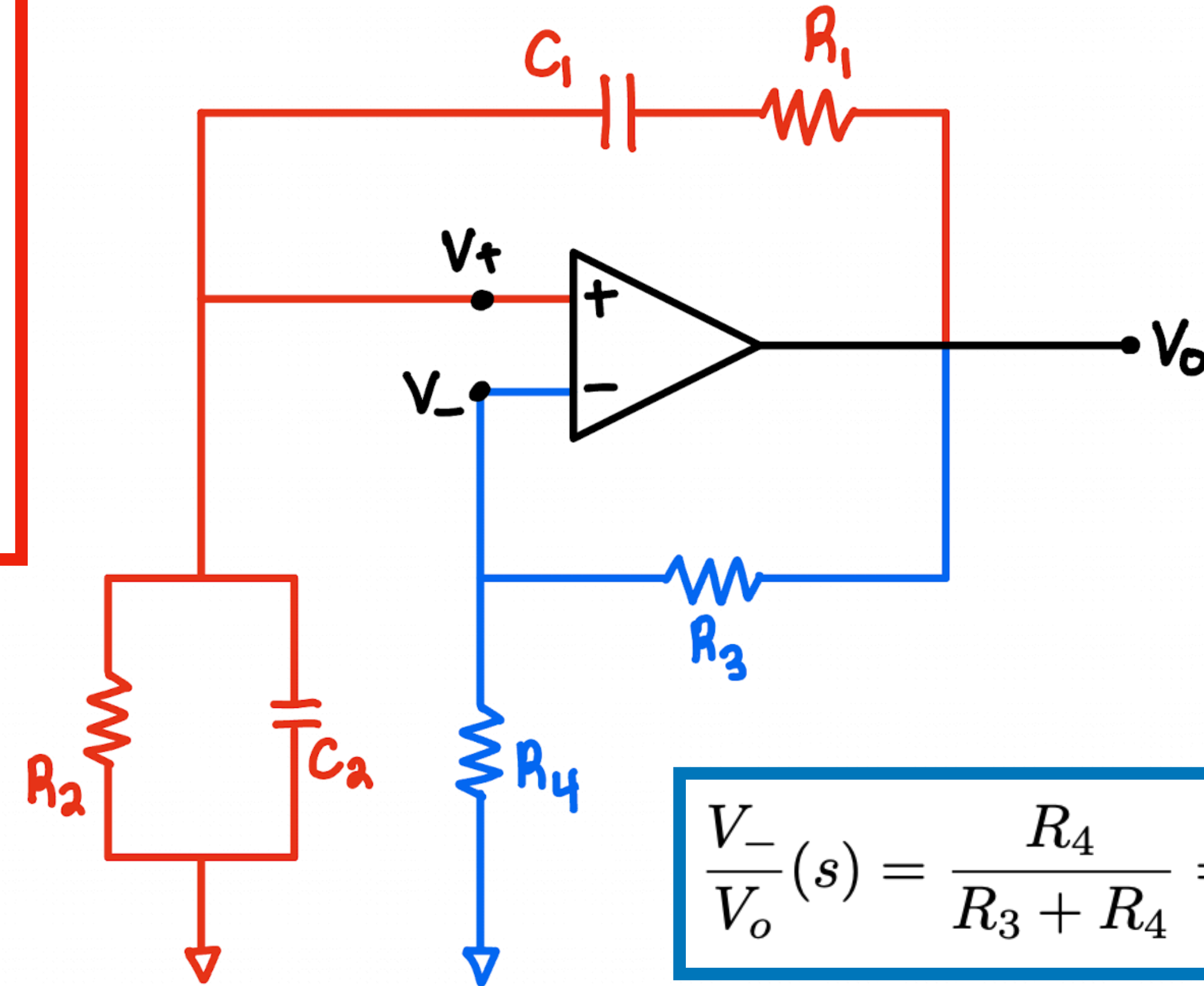
# Wein Bridge Oscillator


$$\begin{aligned}
 \frac{V_+}{V_o}(s) &= \frac{\frac{1}{1/R_2 + 1/\frac{1}{sC_2}}}{R_1 + \frac{1}{sC_1} + \frac{1}{1/R_2 + 1/\frac{1}{sC_2}}} \\
 &= \frac{sR_2C_1}{s^2R_1C_1R_2C_2 + s(R_1C_1 + R_2C_2 + R_2C_1) + 1} \\
 &= \frac{s\tau_{21}}{s^2\tau_1\tau_2 + s(\tau_1 + \tau_2 + \tau_{21}) + 1} \quad (6)
 \end{aligned}$$

$$v_o = A(v_+ - v_-) \Leftrightarrow V_o(s) = A(V_+(s) - V_-(s))$$



$$\frac{V_-}{V_o}(s) = \frac{R_4}{R_3 + R_4} = \frac{1}{G}$$

# Linear Analysis

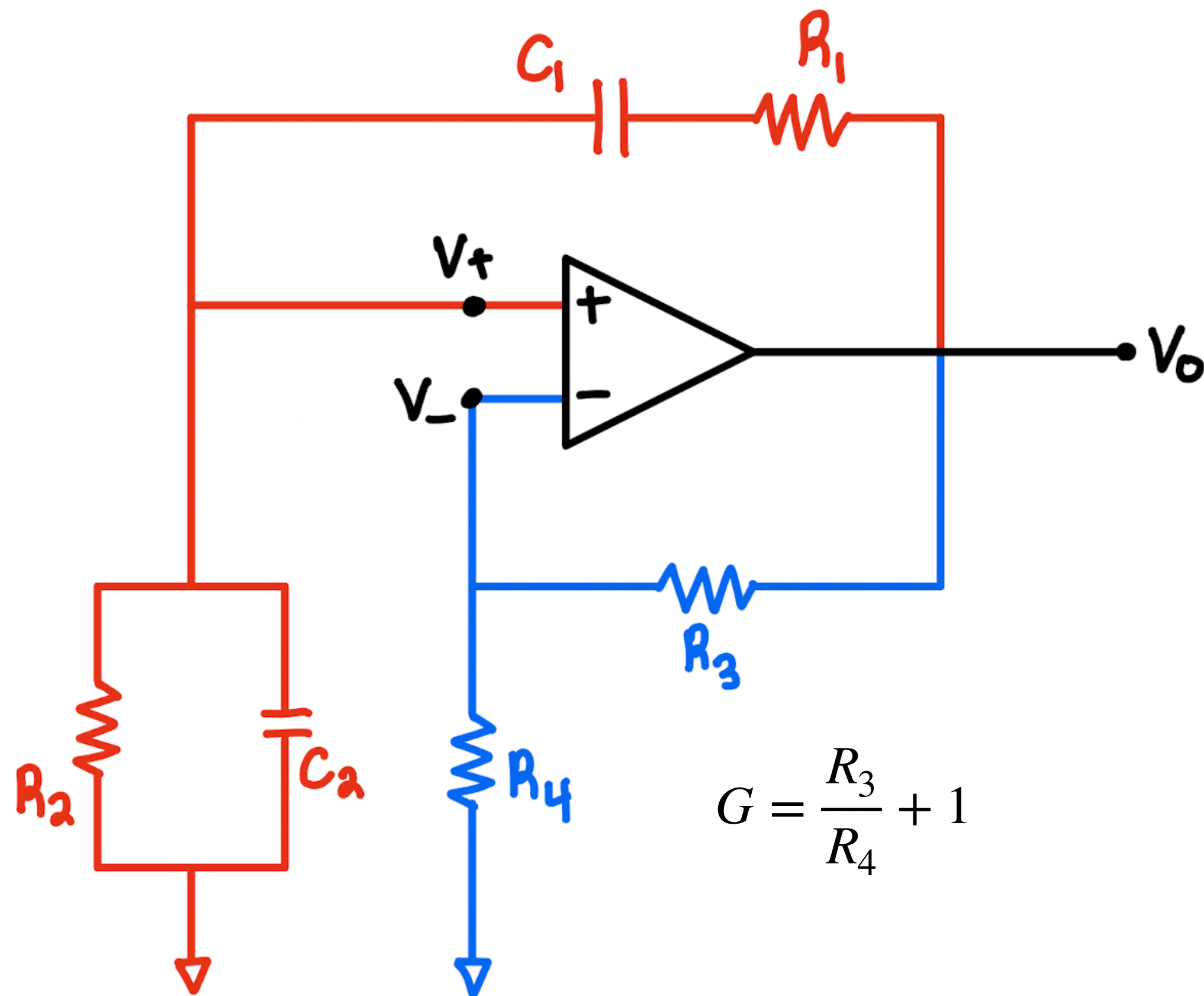

$$V_o = A(V_+ - V_-)$$

$$0 = V_o \left( s^2 \tau_1 \tau_2 + s \left( \tau_1 + \tau_2 + \tau_{21} - \frac{GA}{G+A} \tau_{21} \right) + 1 \right)$$

$$= \tau_1 \tau_2 \ddot{v}_o + \left( \tau_1 + \tau_2 + \tau_{21} - \frac{GA}{G+A} \tau_{21} \right) \dot{v}_o + v_o. \quad (9)$$

$$0 = \frac{1}{\omega_n^2} \ddot{x} + \frac{2\zeta}{\omega_n} \dot{x} + x.$$

$$x(t) = A_0 e^{-\omega_n \zeta t} \sin \left( \omega_n \sqrt{\zeta^2 - 1} t + \phi_0 \right)$$


for constant-amplitude oscillations

$$0 = \tau_1 + \tau_2 + \tau_{21} - \frac{G_* A}{G_* + A} \tau_{21}$$

$$= \tau_1 + \tau_2 + \tau_{21} - G_* \tau_{21} \text{ for } A \gg G_*$$



$$\Rightarrow G_* = \frac{\tau_1 + \tau_2}{\tau_{21}} + 1$$

# Hardware Experiment

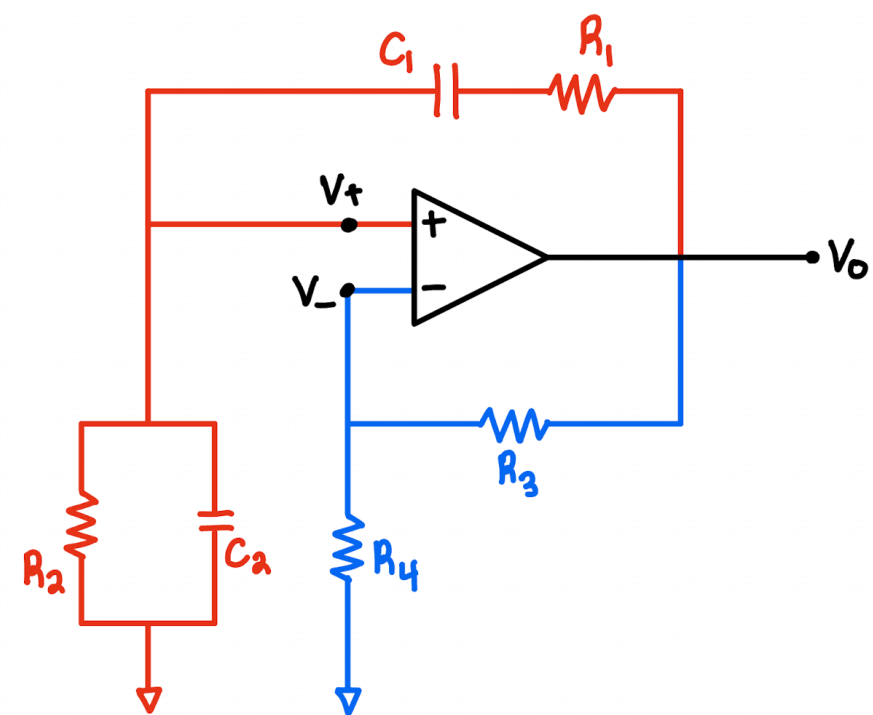


component	value
$R_1$	47 k $\Omega$
$C_1$	68 nF
$R_2$	47 k $\Omega$
$C_2$	68 nF
$R_3$	20 k $\Omega$
$R_4$	10 k $\Omega$

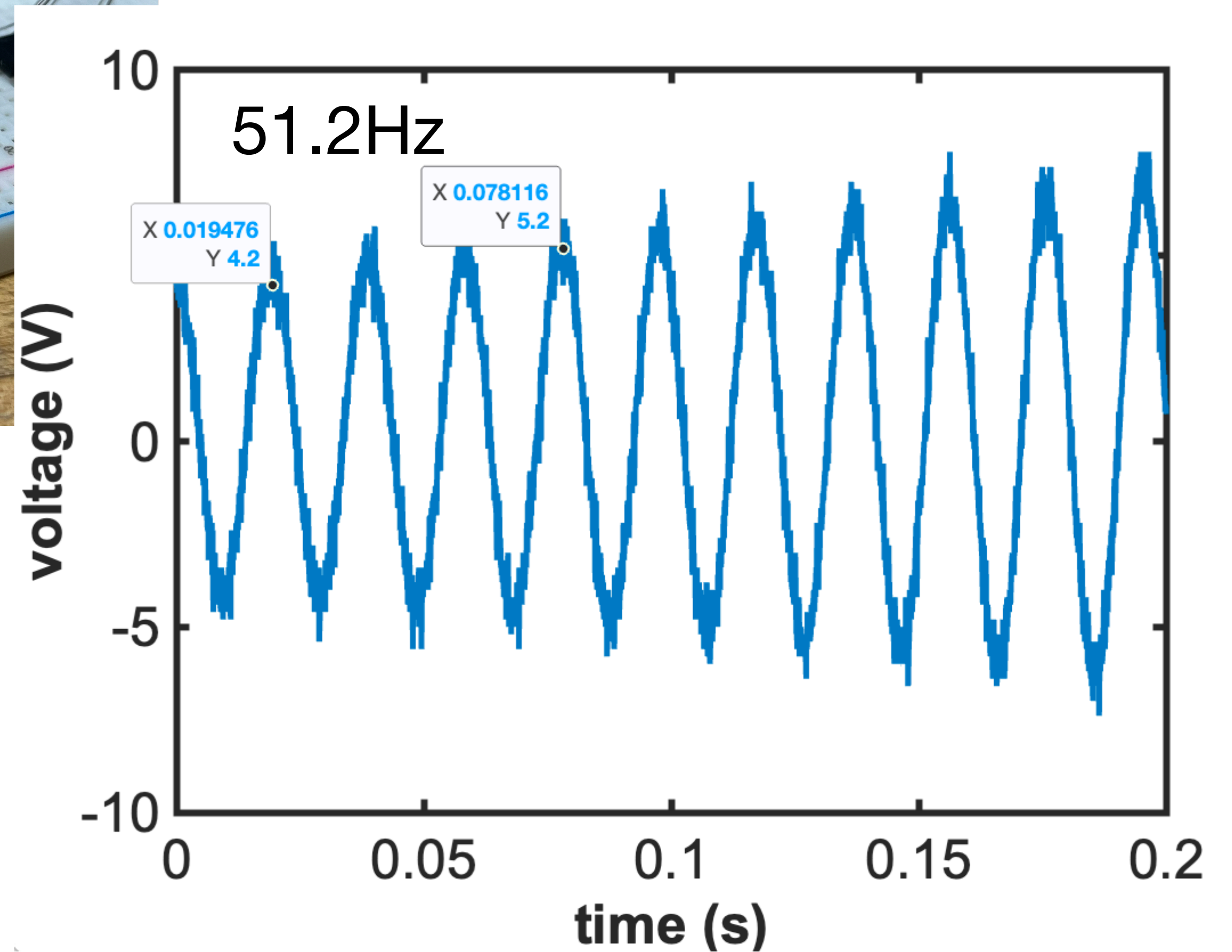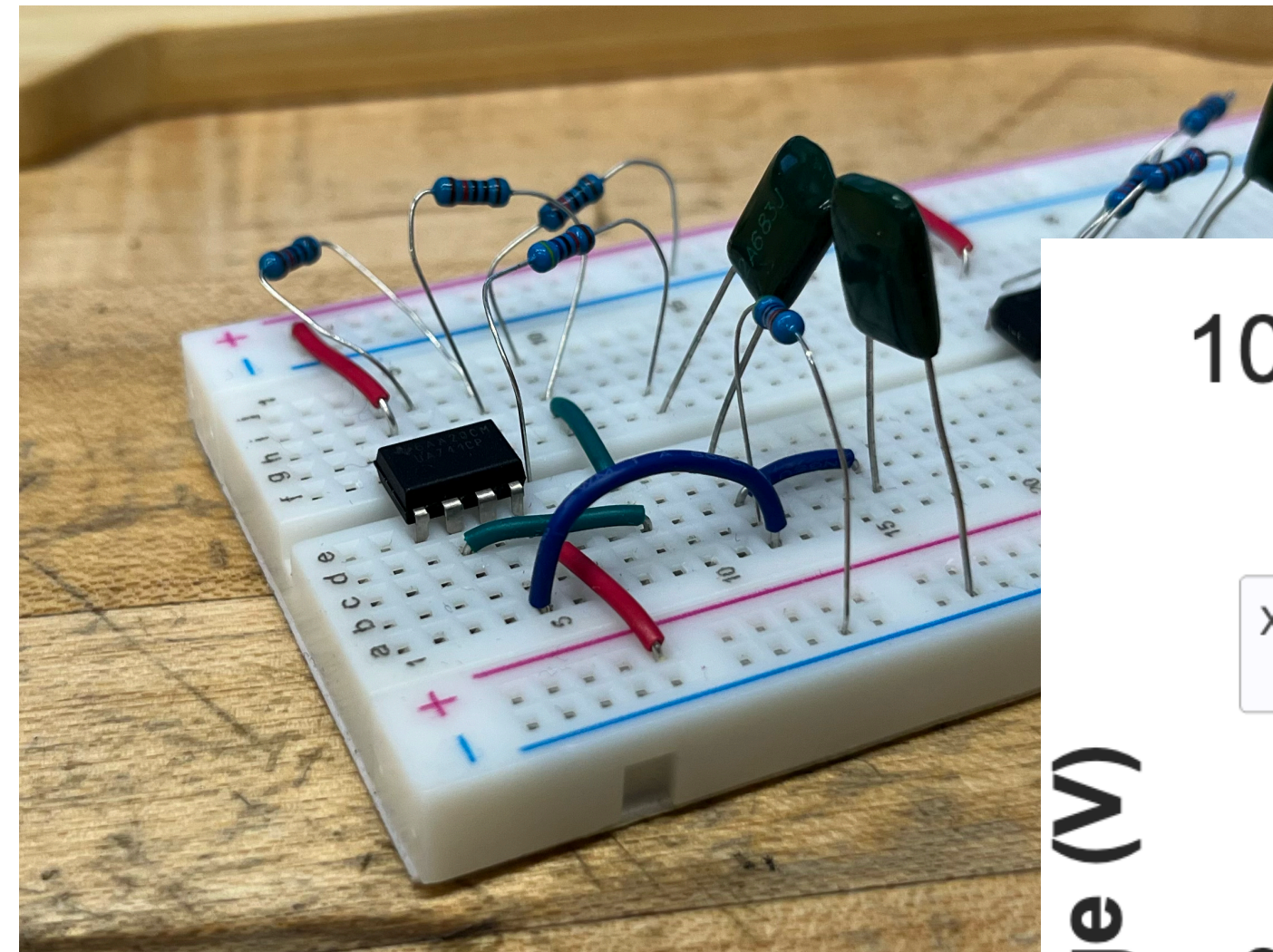
$$\zeta = 0; \omega_n = \omega_d = 49.8\text{Hz}$$




# Component Tolerances

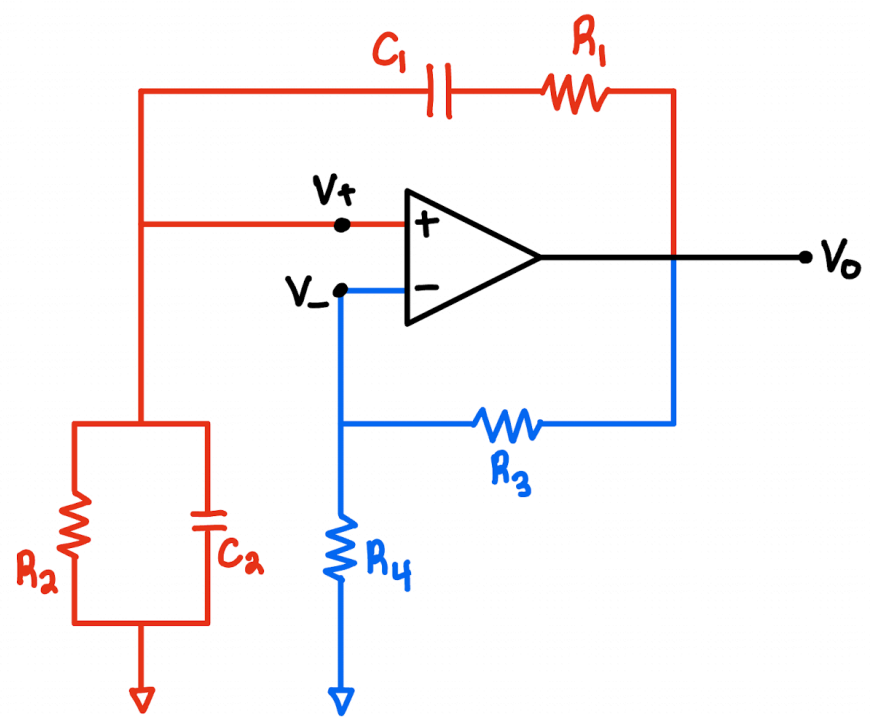

component	nominal value	
R <sub>1</sub>	47 kΩ	
C <sub>1</sub>	68 nF	
R <sub>2</sub>	47 kΩ	
C <sub>2</sub>	68 nF	
R <sub>3</sub>	15kΩ	14.77kΩ
R <sub>4</sub>	8kΩ	8.082kΩ

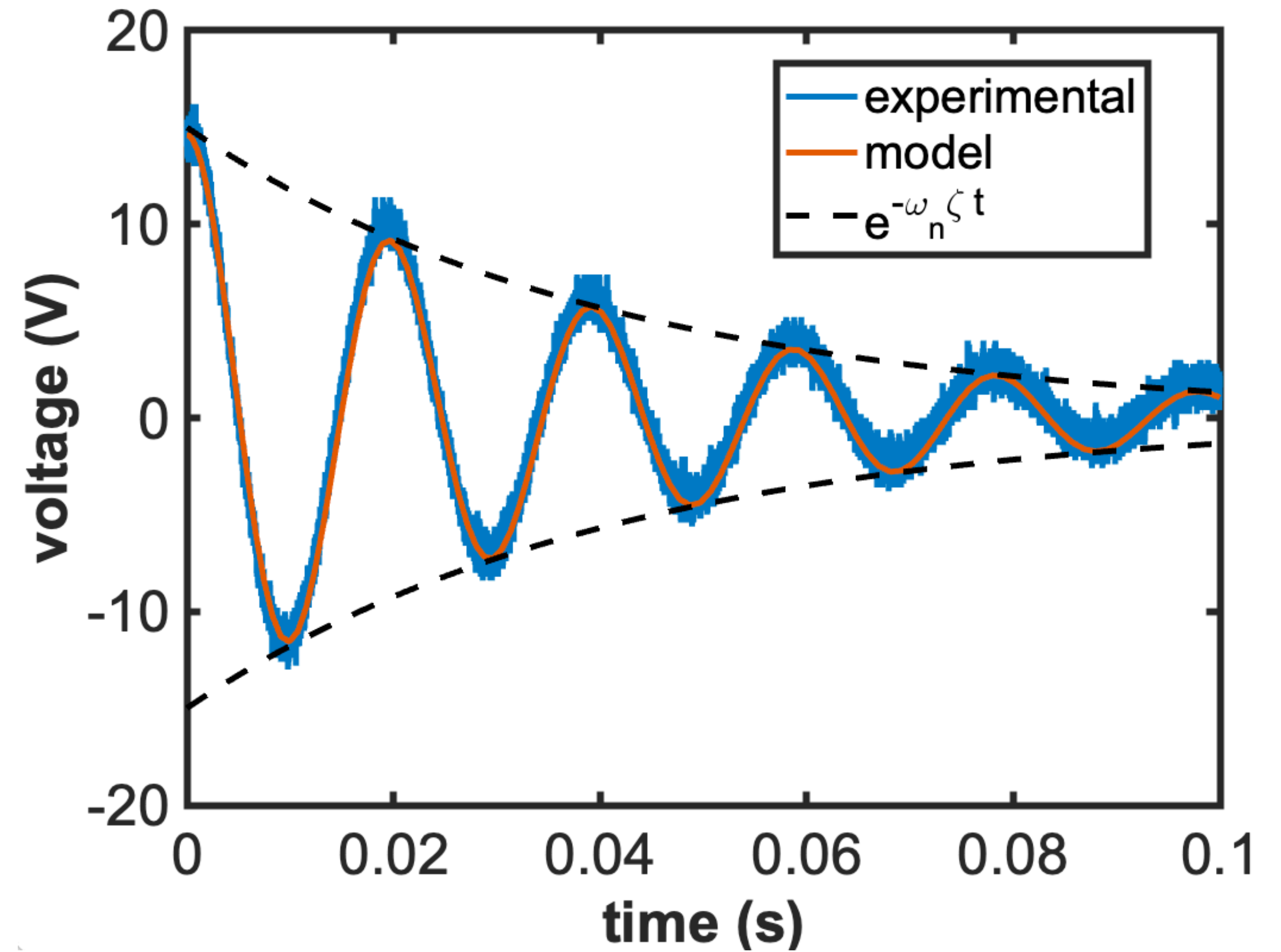

# Unintentional Nonlinearity: Saturation

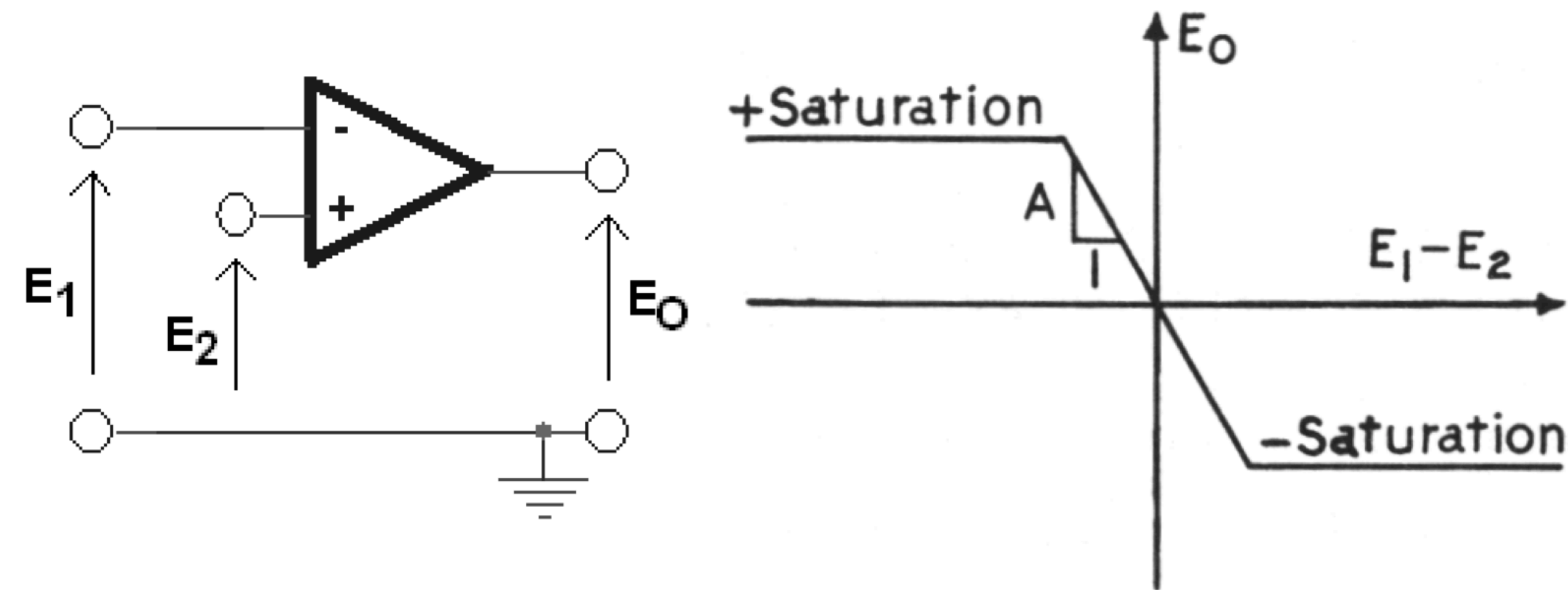


$$s(x) = x (1 - \sigma(-(x - X_l))\sigma(-x) - \sigma(x - X_u)\sigma(x)) + 500 ((X_l - x)\sigma(-(x - X_l)) + (X_u - x)\sigma(x - X_u))$$

$\sigma(x)$  = smooth step function  $\frac{1}{1+e^{-100x}}$

$X_l$  = lower saturation bound

$X_u$  = upper saturation bound




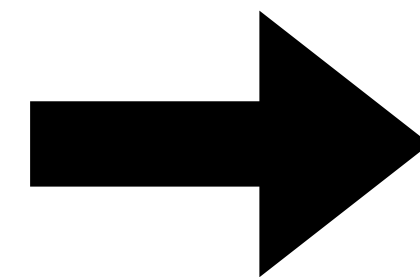
$$\begin{cases} \dot{v}_o = \dot{v}_o \\ \ddot{v}_o = -\frac{(\tau_1 + \tau_2 + \tau_{21} - G\tau_{21})\dot{v}_o + v_o}{\tau_1\tau_2} \end{cases}$$



$$\begin{cases} \dot{v}_o = s(\dot{v}_o) \\ \ddot{v}_o = -\frac{(\tau_1 + \tau_2 + \tau_{21} - G\tau_{21})\dot{v}_o + v_o}{\tau_1\tau_2} \end{cases}$$
 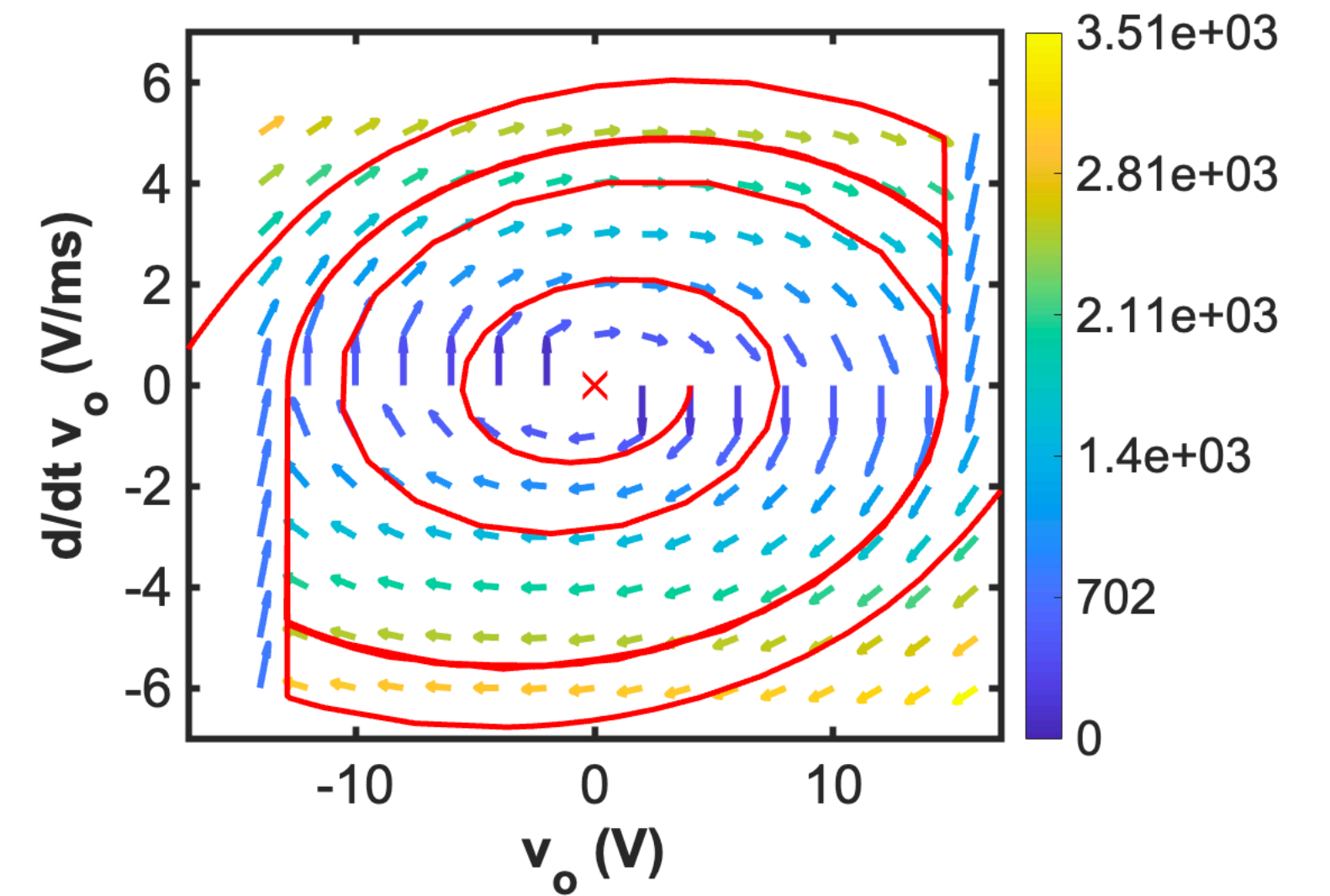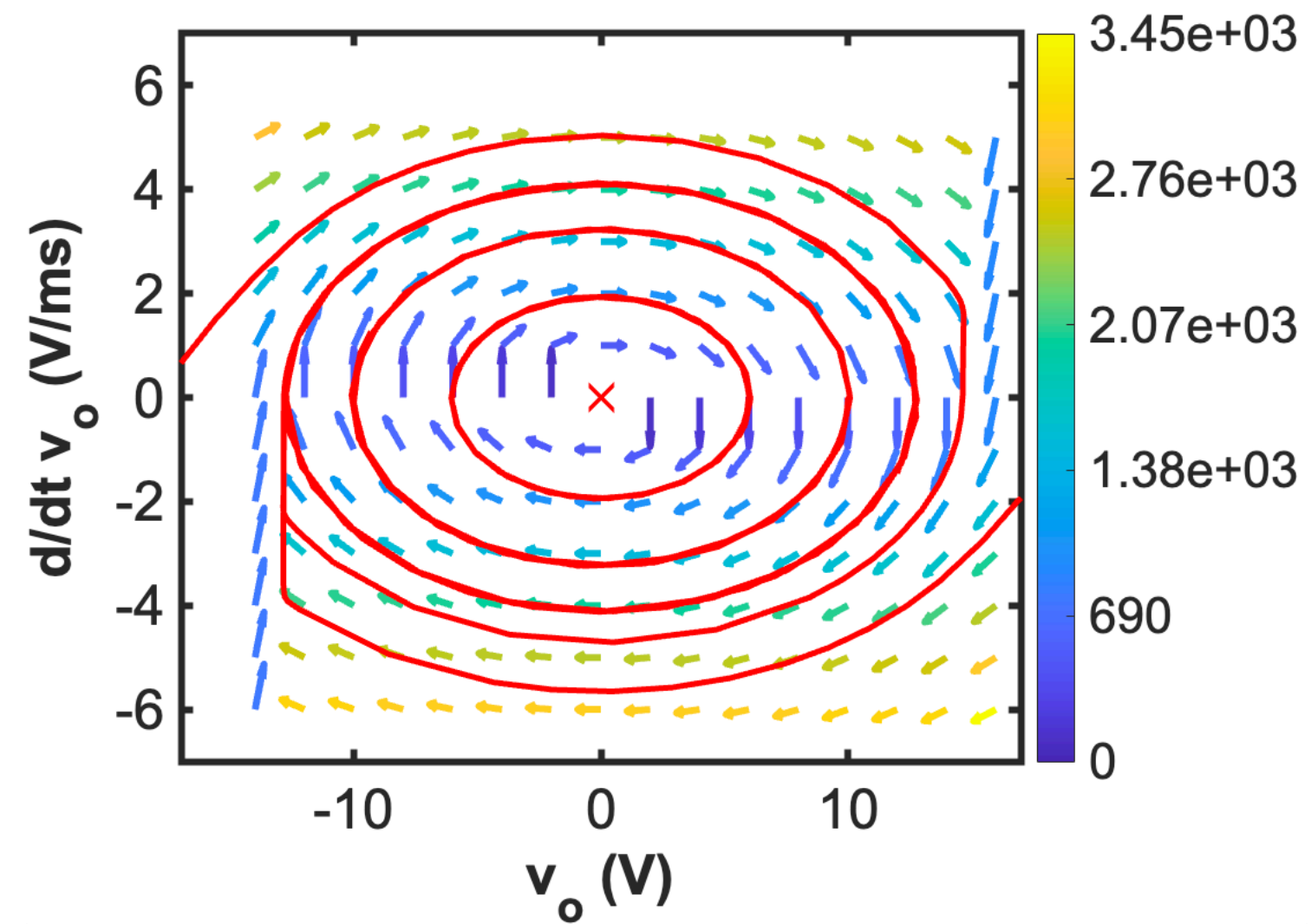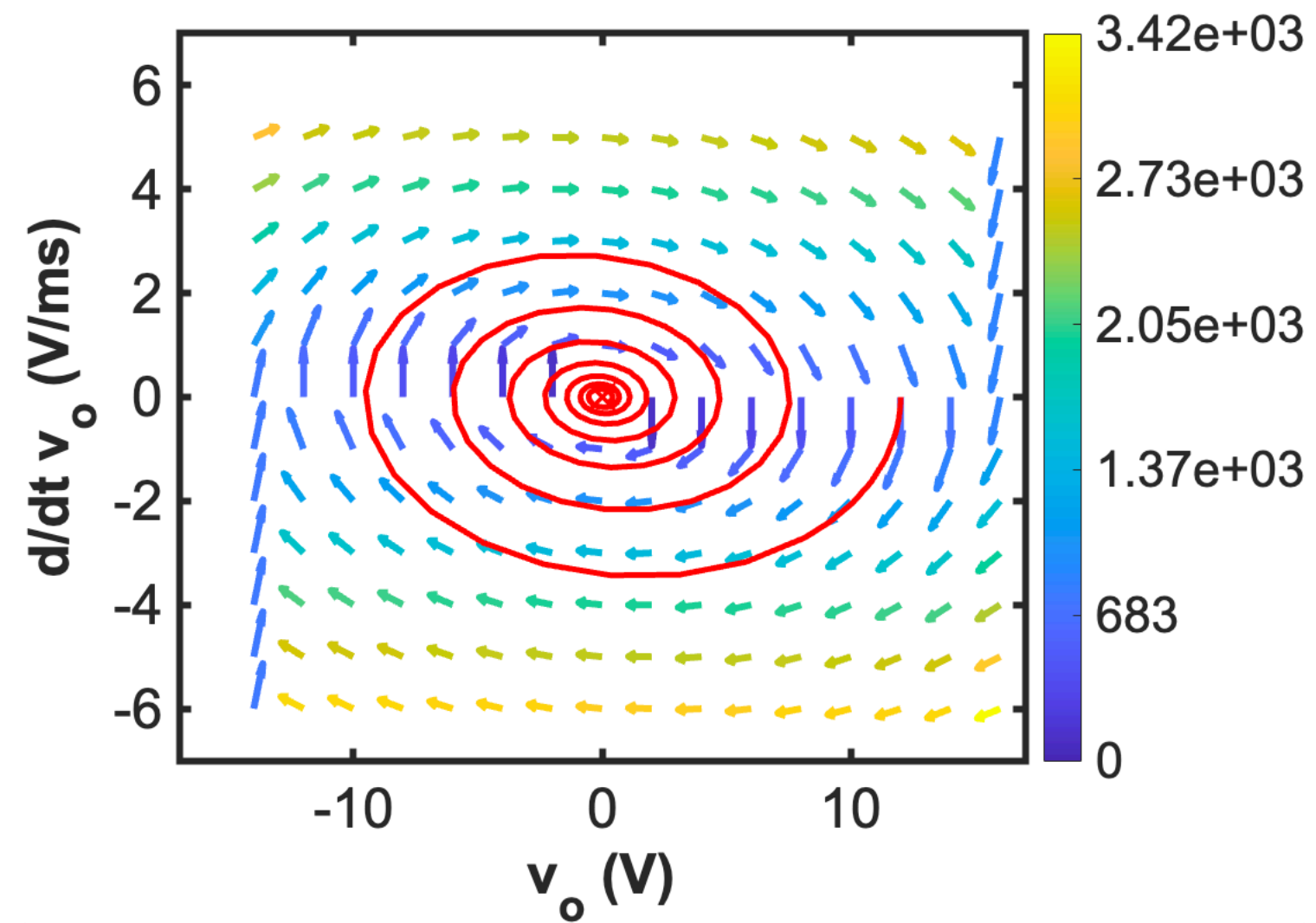
# G as a Parameter

$$G_* = \frac{\tau_1 + \tau_2}{\tau_{21}} + 1$$






$G_*$


degenerate Hopf Bifurcation



# Hardware Experiment

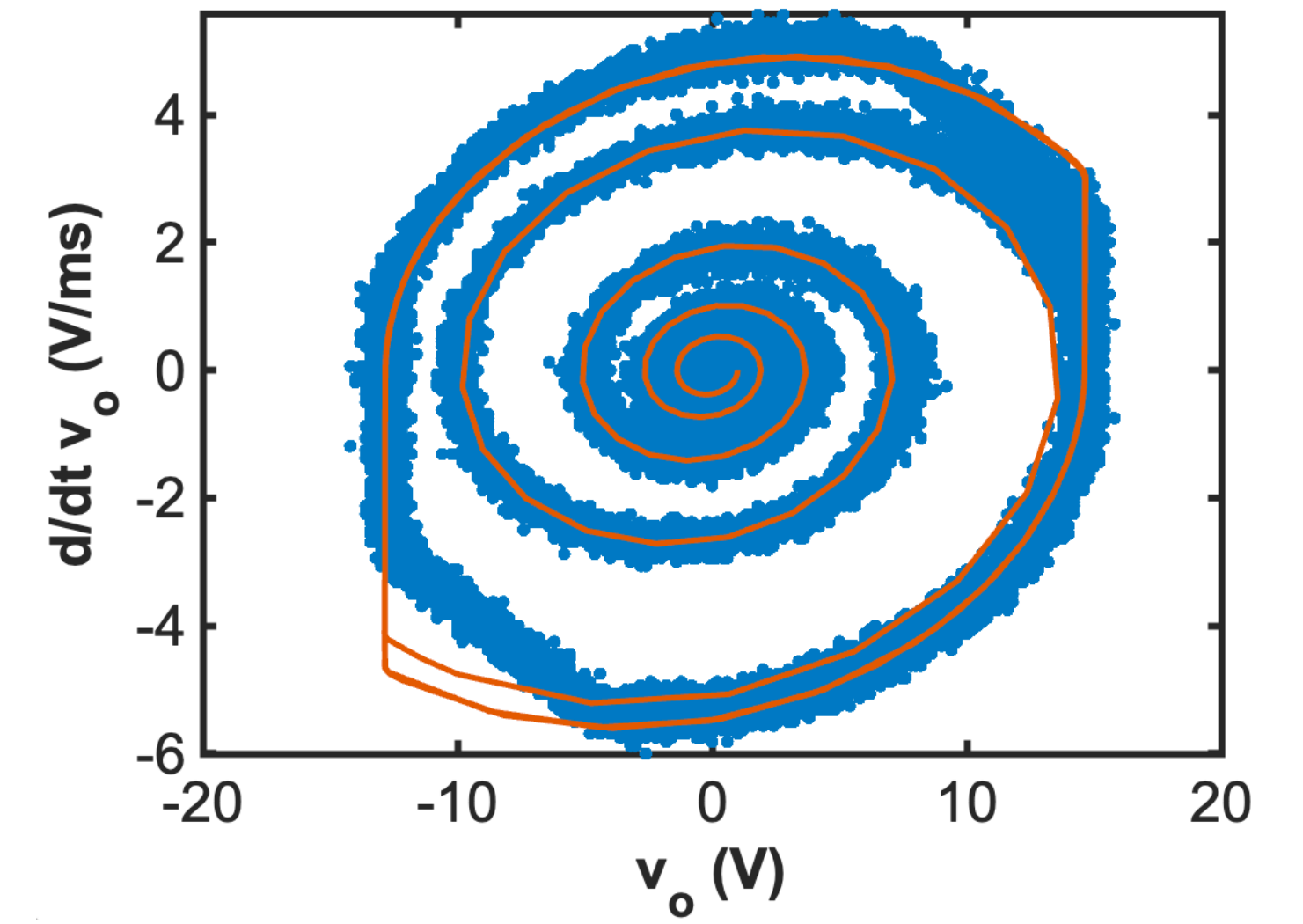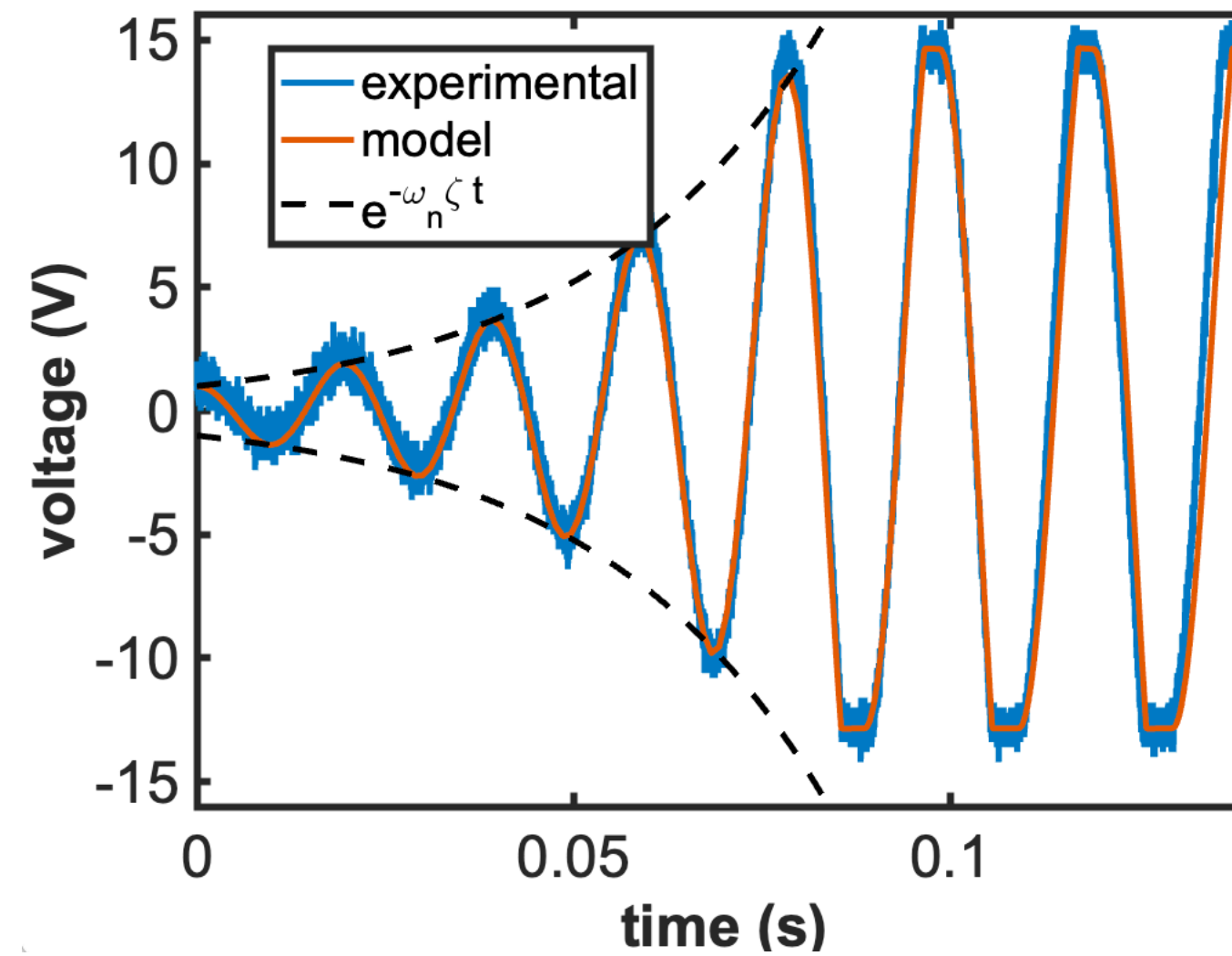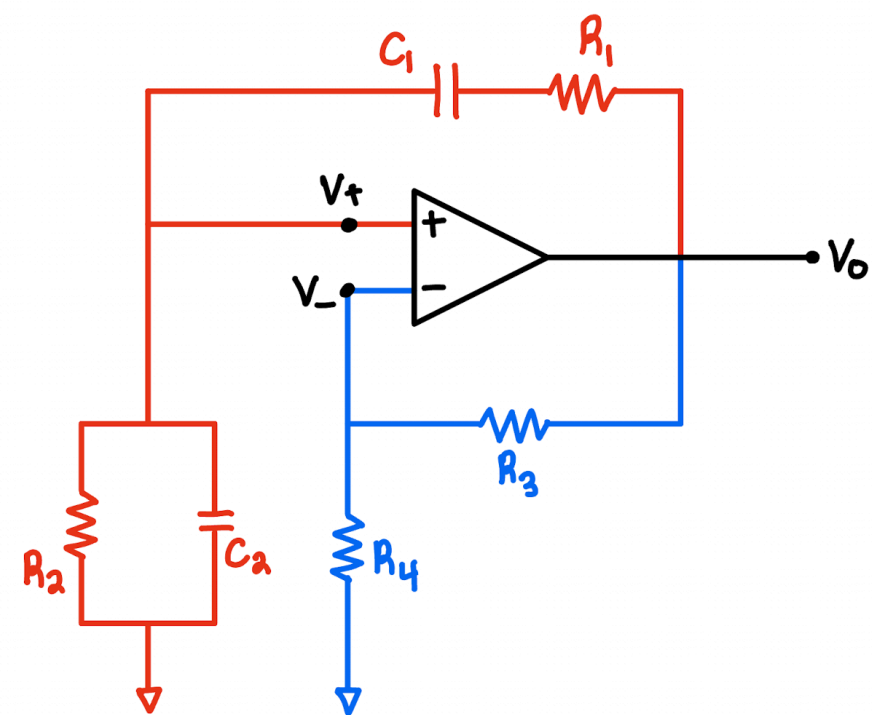

component	nominal value	measured value
R <sub>1</sub>	47 kΩ	46.54 kΩ
C <sub>1</sub>	68 nF	68.12 nF
R <sub>2</sub>	47 kΩ	46.14 kΩ
C <sub>2</sub>	68 nF	65.93 nF
R <sub>3</sub>	22 kΩ	21.52 kΩ
R <sub>4</sub>	10 kΩ	9.875 kΩ

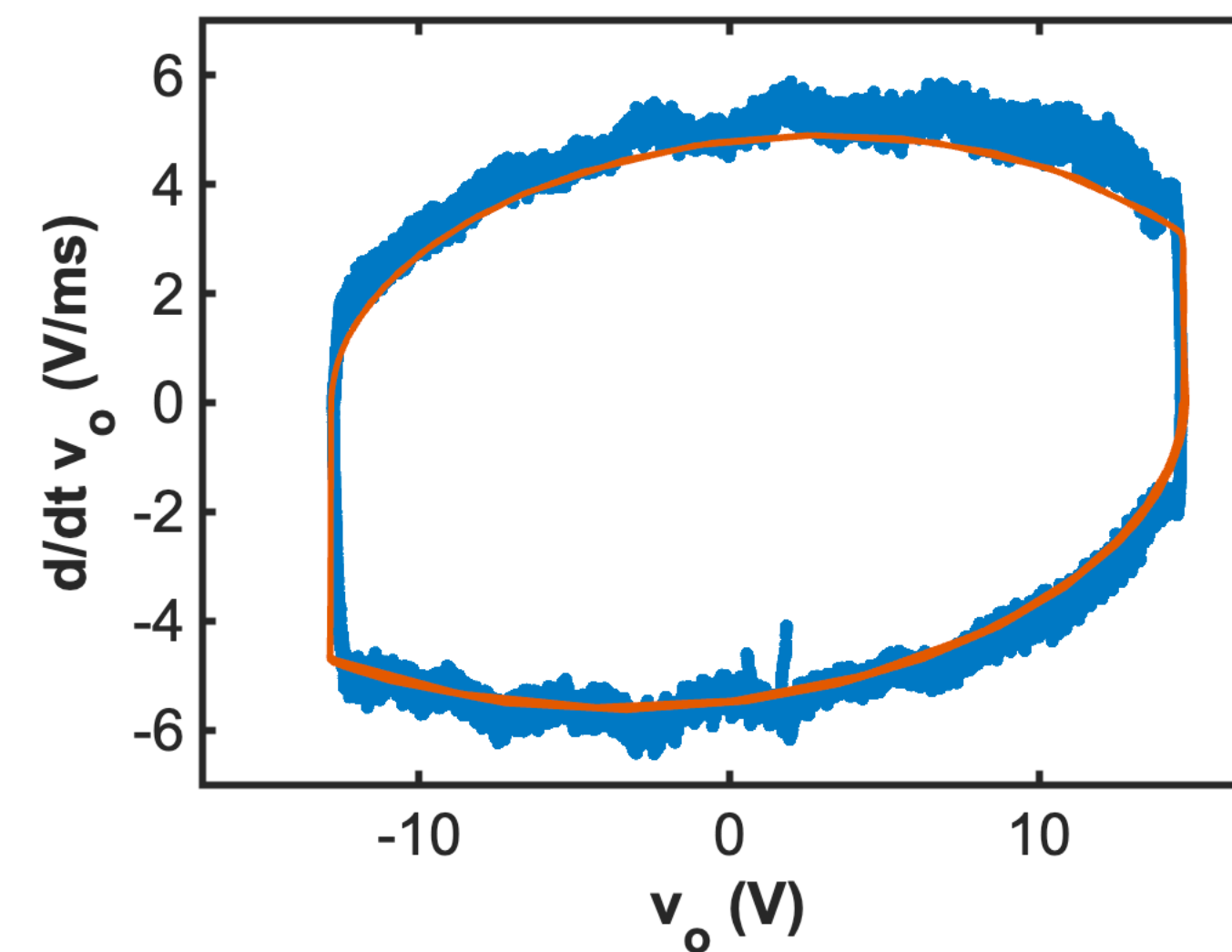

# Nonlinear Feedback

$$0 = \tau_1 \tau_2 \dot{v}_o + (\tau_1 + \tau_2 + \tau_{21} \textcircled{G} - 1) \dot{v}_o + v_o$$

function of oscillation amplitude?

$$G = \frac{R_3}{\textcircled{R_4}} + 1$$

increase when amplitude is too high  
decrease when amplitude is too low



more voltage  $\rightarrow$  more heat  
more heat  $\rightarrow$  more resistance  
more resistance  $\rightarrow$  lower gain  
(and vice versa)

# Lightbulb Constitutive Equations

$$R(T) = R_0(1 + \alpha(T - T_0)) \quad (14)$$

where:

$T$  = temperature (K)

$\alpha$  = temperature coefficient of resistance ( $\Omega/\text{K}$ )

$T_0$  = room temperature (measured to be 295K)

$R_0$  = resistance ( $\Omega$ ) measured at room temperature

$$mc\dot{T} = \frac{v_R^2}{R(T)} - Q(T). \quad (15)$$

where:

$m$  = mass of filament (kg)

$c$  = specific heat of filament (J/kgK)

$v_R$  = voltage (V) across resistor

$Q$  = heat emitted by bulb (W)

$$Q(T) = \epsilon\sigma A_s(T^4 - T_0^4). \quad (16)$$

where:

$\epsilon$  = thermal emissivity coefficient

$\sigma$  = Steffan-Boltzmann constant ( $\text{W}/\text{m}^2\text{K}^4$ )

$A_s$  = surface area of filament ( $\text{m}^2$ )

# Replacing $R_4$ with $R(T)$

$$\begin{cases} \dot{v}_o = \dot{v}_o \\ \ddot{v}_o = -\frac{(\tau_1 + \tau_2 + \tau_{21} - G(T)\tau_{21})\dot{v}_o + v_o}{\tau_1\tau_2} \\ \dot{T} = \frac{1}{mc} \left( \frac{R(T)}{(R_3 + R(T))^2} v_o^2 - Q(T) \right). \end{cases} \quad \begin{cases} v_o = Ae^{-\omega_n \zeta t} \sin(\omega_d t + \phi(t)) \\ \langle v_o \rangle = \frac{1}{\sqrt{2}} A \end{cases}$$

$$G(T) = 1 + \frac{R_3}{R(T)}$$

↓ reduced model ↓

$$\begin{cases} \dot{A} = -\zeta(T)\omega_n A \\ \dot{T} = \frac{1}{mc} \left( \frac{R(T)}{(R_3 + R(T))^2} \frac{A^2}{2} - Q(T) \right) \end{cases}$$

$$\omega_n = \frac{1}{\sqrt{\tau_1\tau_2}}; \zeta(T) = \frac{\omega_n}{2} (\tau_1 + \tau_2 + (1 - G(T))\tau_{21}),$$

# Steady-state Coefficient Fitting

$$mc\dot{T} = \frac{v_R^2}{R(T)} - Q(T)$$

$$Q(T) = \epsilon\sigma A_s (T^4 - T_0^4)$$


$$R(T) = R_0(1 + \alpha(T - T_0))$$

$$\dot{T} = 0 \implies v_R = \sqrt{R(T)Q(T)}$$


$$R_0 = 1.35\Omega$$

$$\alpha = .0132$$


$$\epsilon A_s = 1.692 \cdot 10^{-4}$$

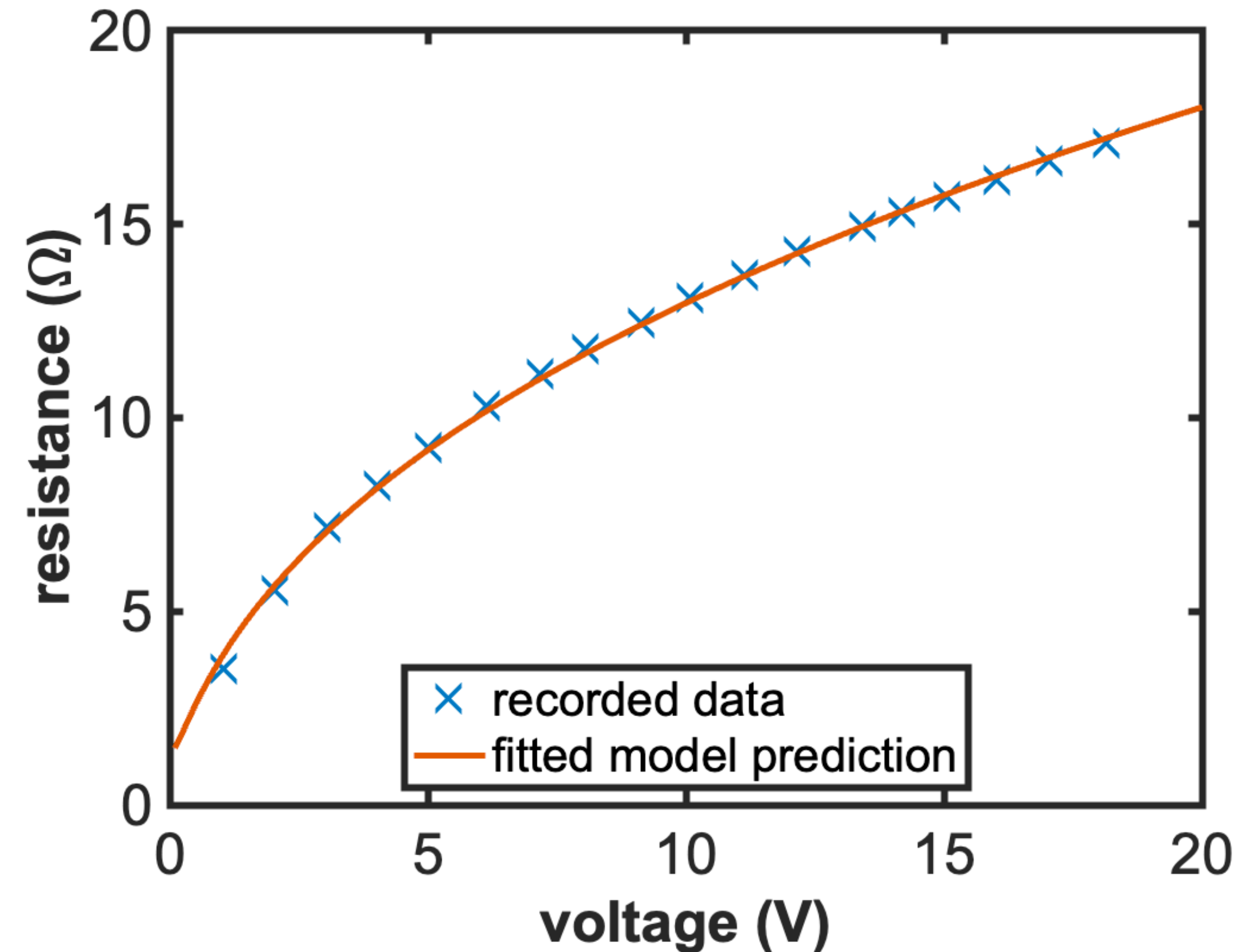


# Effect of $mc$

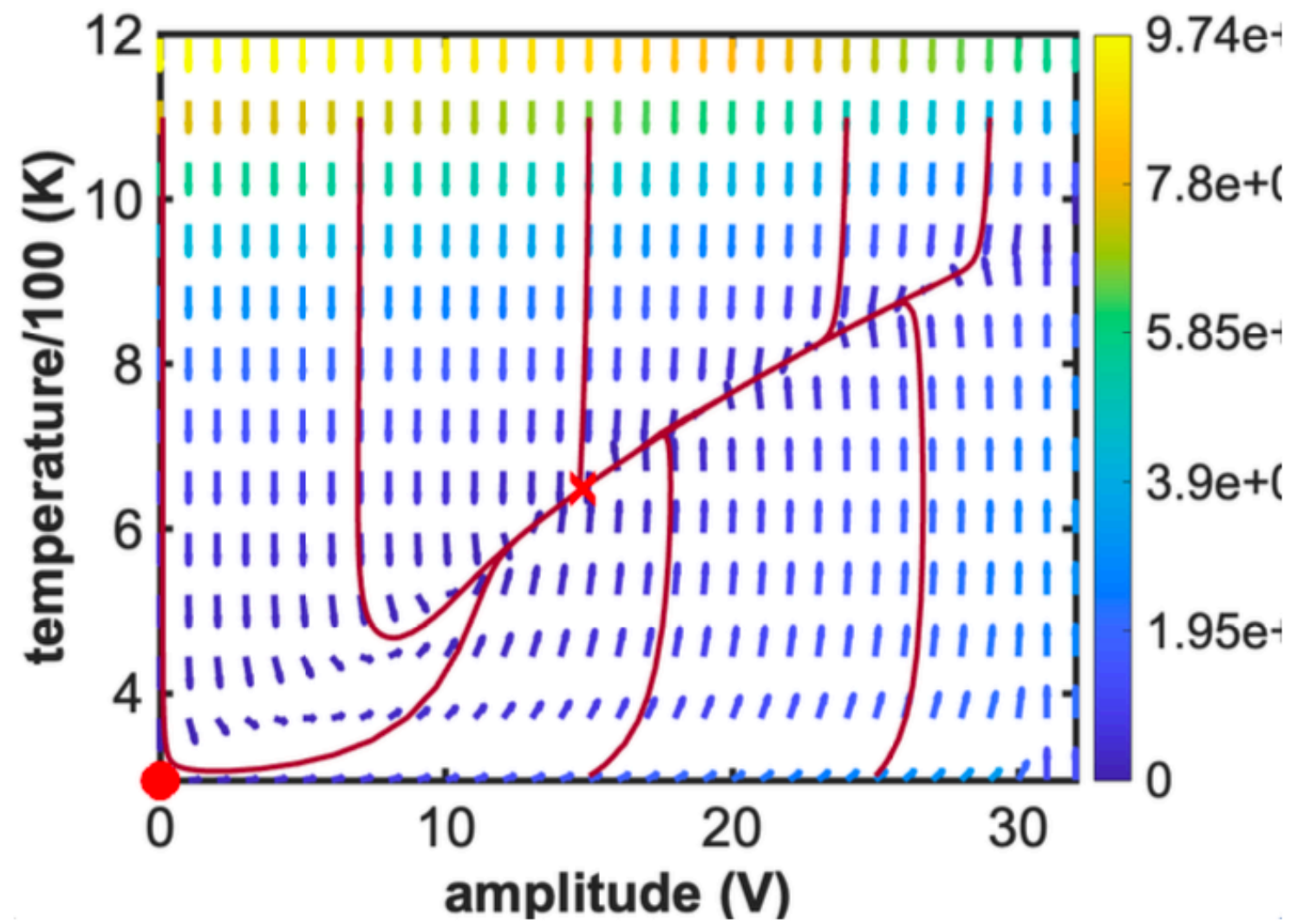

(a)  $mc = 10^{-6}$

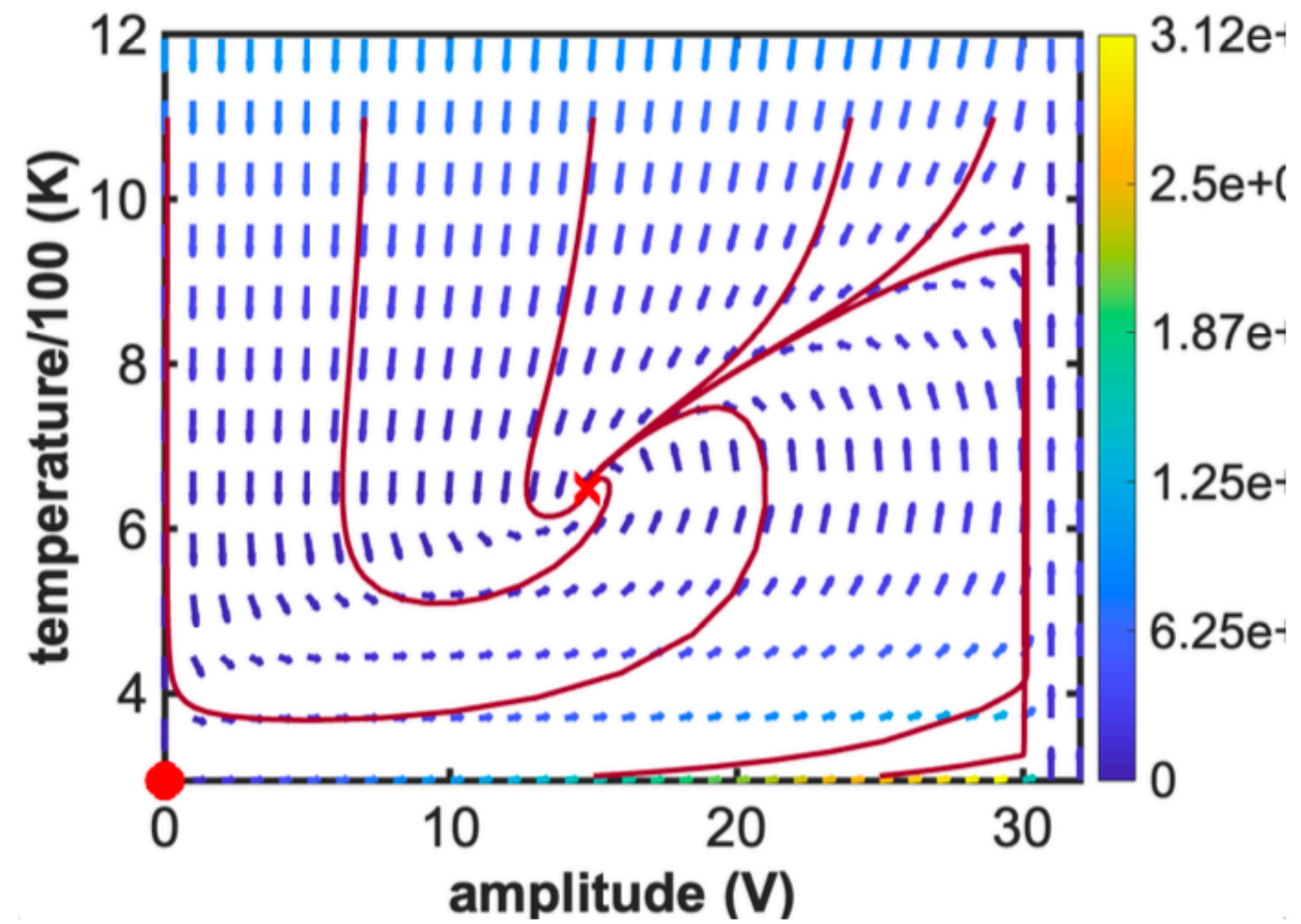



(b)  $mc = 10^{-5}$

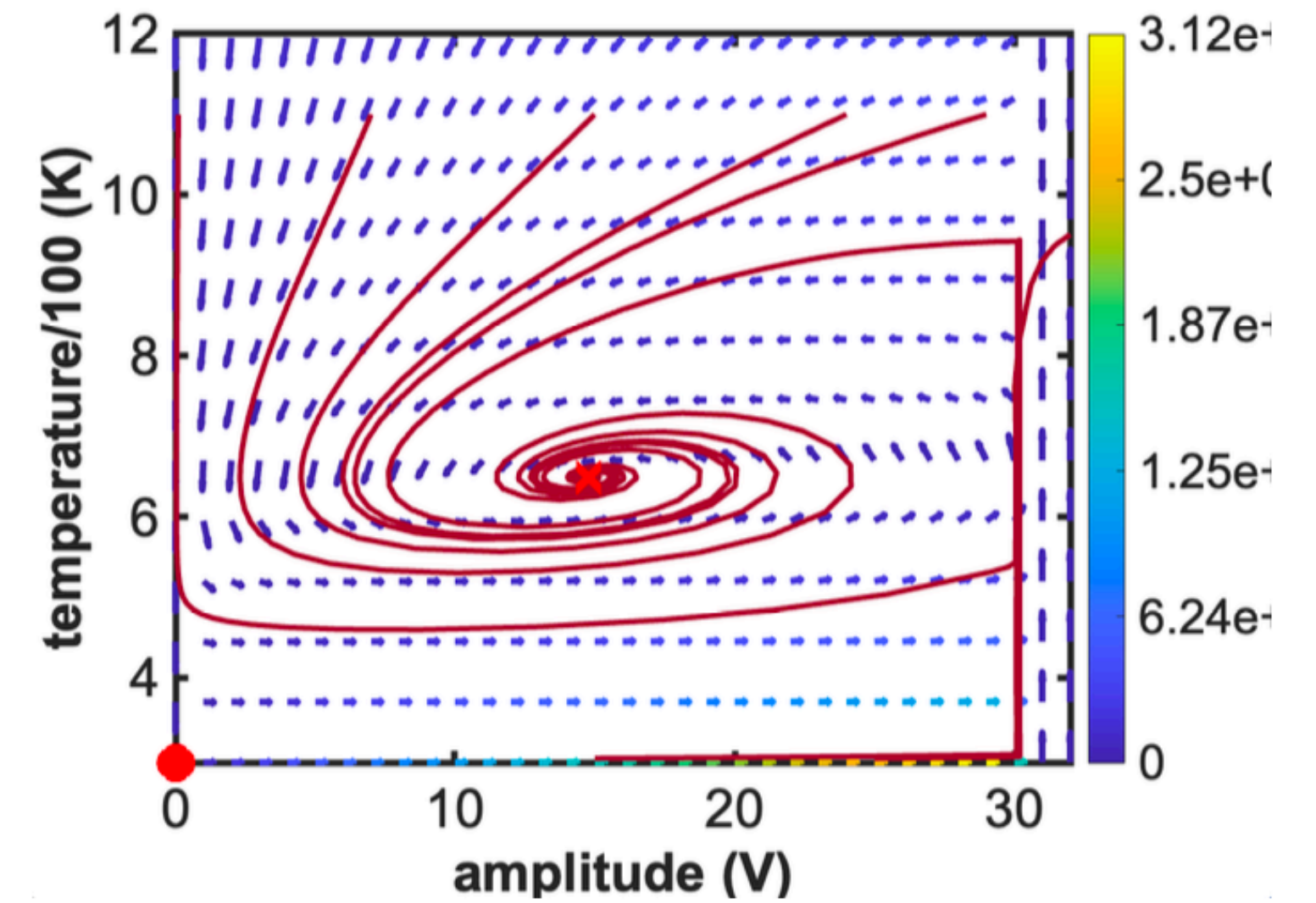


(c)  $mc = 10^{-4}$

# R<sub>4</sub> as a Parameter


$$G(T) = 1 + \frac{R_3}{R(T)}$$

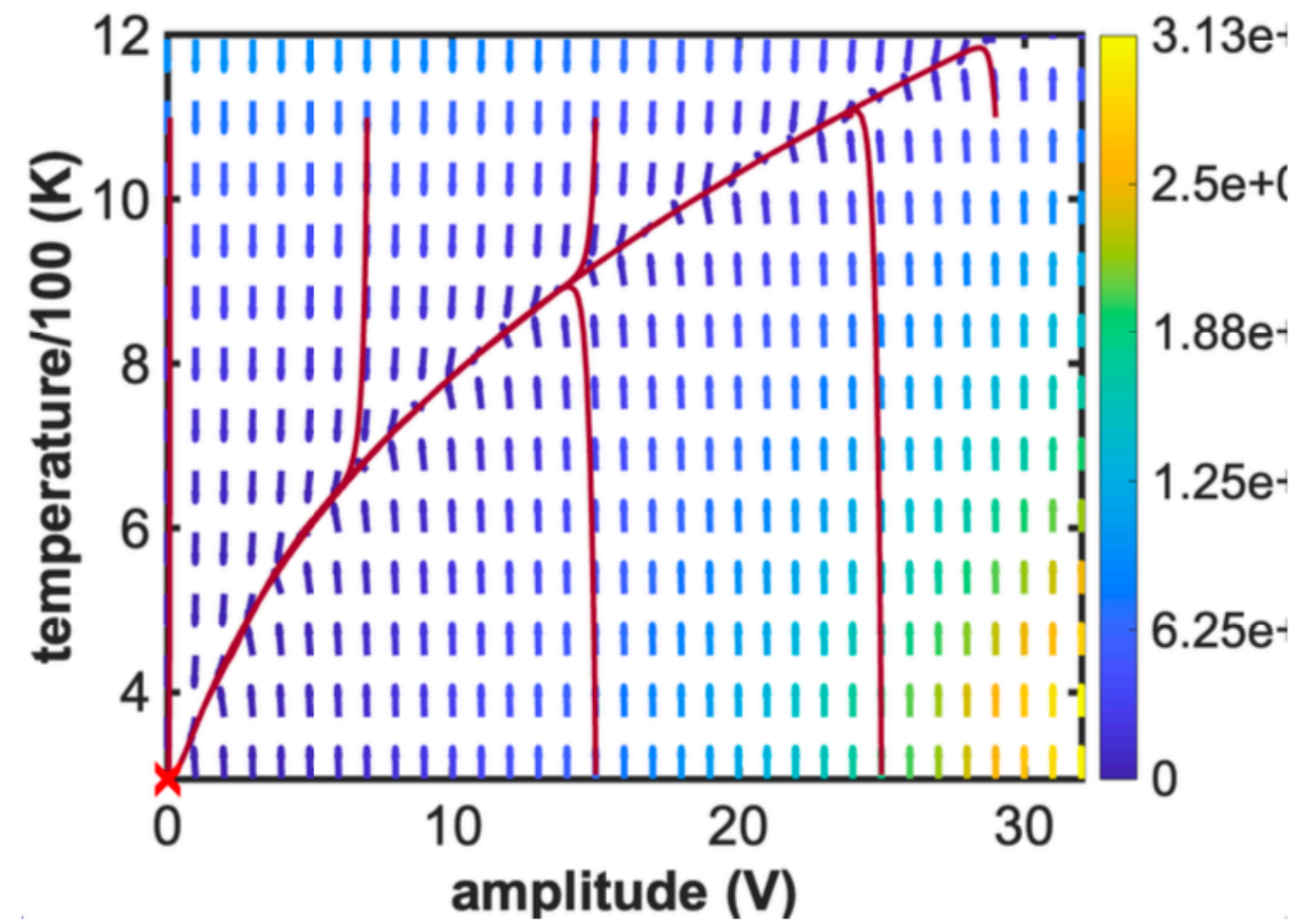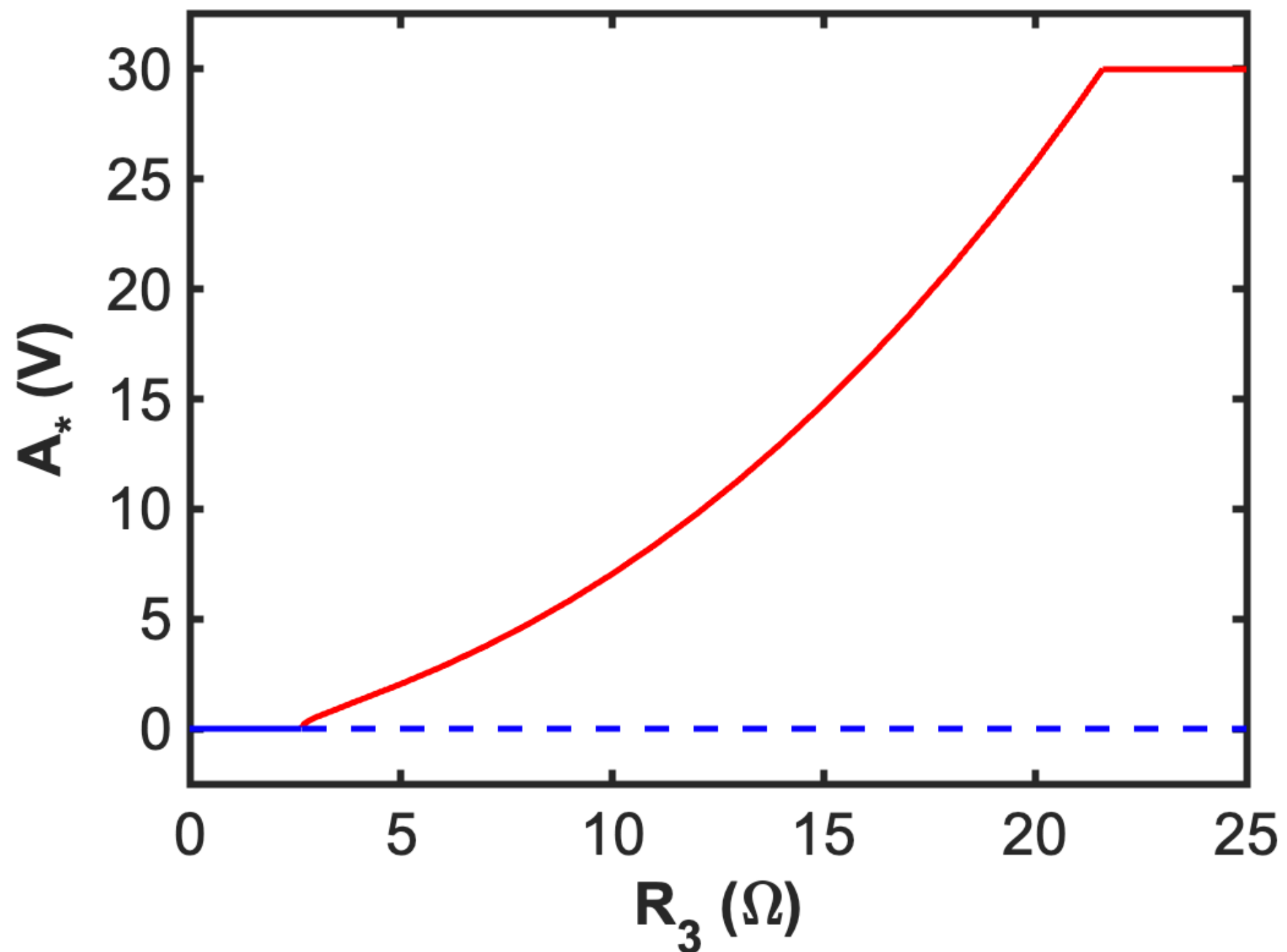


(a)  $R_3 = 2 \Omega$

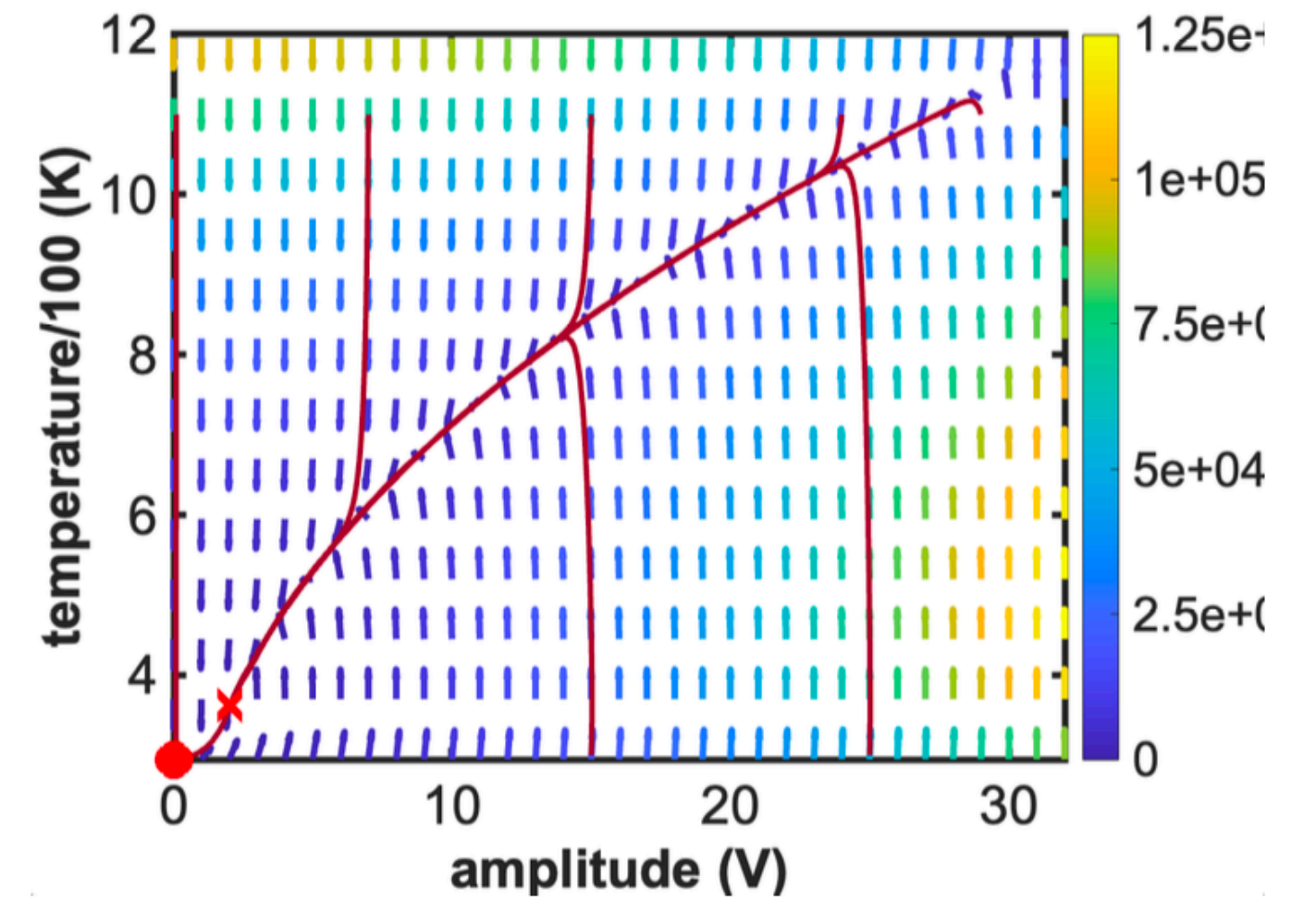

(b)  $R_3 = 5 \Omega$

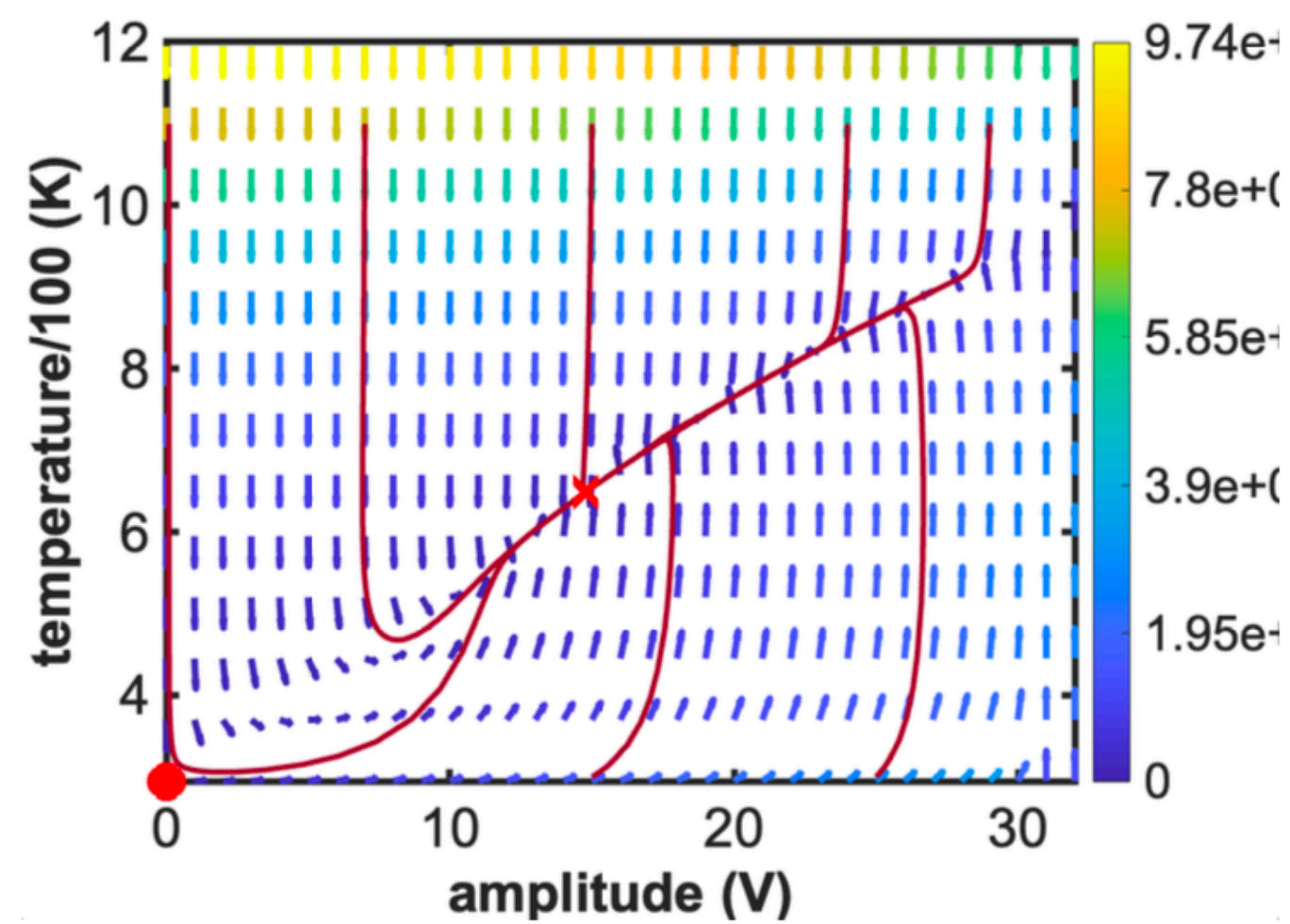

(c)  $R_3 = 15 \Omega$

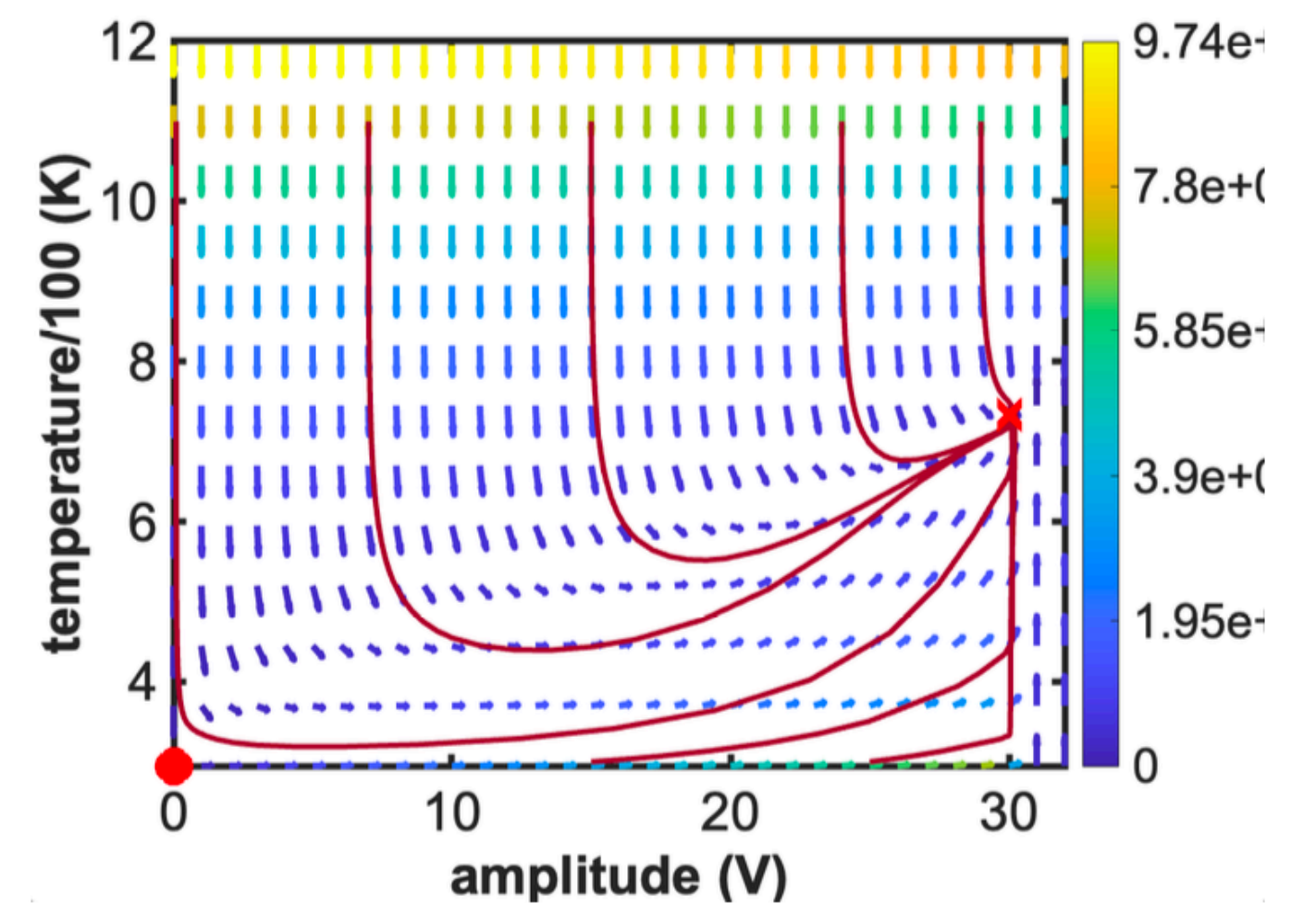

(d)  $R_3 = 30 \Omega$

# Experimental Validation

